






Simulator time: 00:00:04



Code

Stop Simulation

Send To

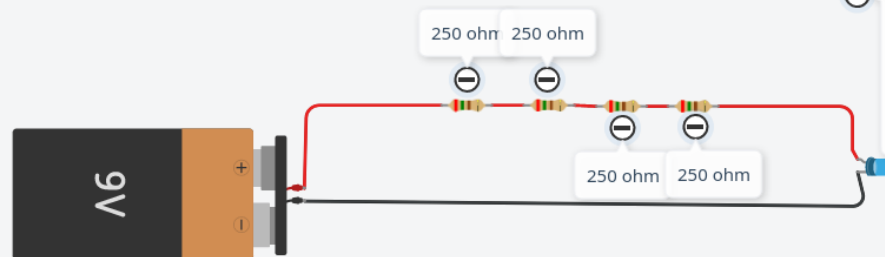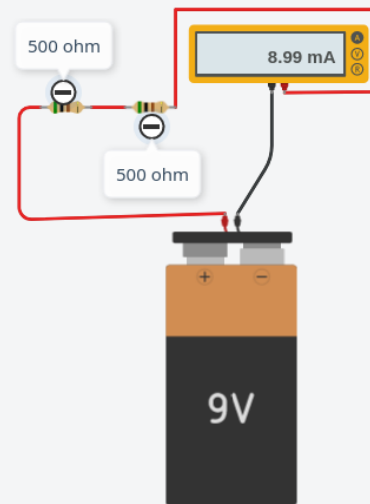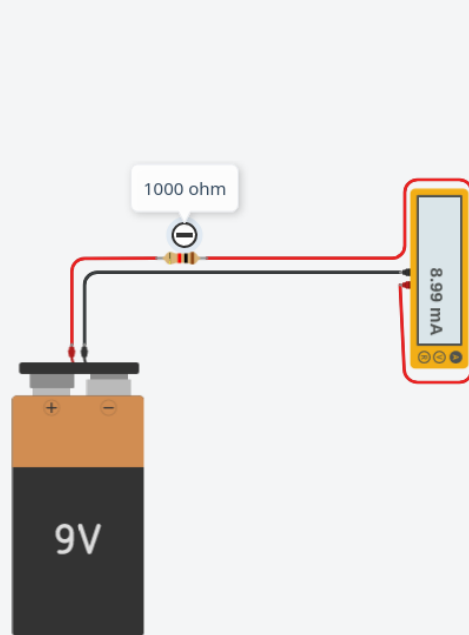

Ques 1: Build a series circuit with a 9V battery and a 1000 ohm resistor (9mA current flow)

Solution:-

V stands for Voltage the standard unit of voltage is V(volt)

I stands for Current and the standard unit of current is A(Ampere) or mA(milliampere)

R is Resistance and the standard unit of R

V= 9V(given)

R= 1000 ohm (given)

The current flow in the circuit is 9mA.

According to ohms law:

$R = V/I$

$I = V/R$

$I = 9/1000$

$I = 9mA$ (1mA = 0.001A)

Build a series circuit with a 9V and 1000 ohm resistance

$R(s) = R1 + R2$

let the two resistance be equal to R

$R(s) = R + R$

$1000 = 2R$

$1000/2 = R$

$500 = R$

$R = 500 \text{ ohm}$

$R1 = R2 = R = 500 \text{ ohm}$

Then, the resistance will be $R1 = 500\text{ohm}$ and $R2 = 500 \text{ ohm}$

If, I connect four Resistance in series then one resistance will be equal to 250 ohm


$R(s) = R1 + R2 + R3 + R4$

$R(s) = 4R$

$1000 = 4R$

$R = 250 \text{ ohm}$

$R = R1 = R2 = R3 = R4 = 250\text{ohm}$

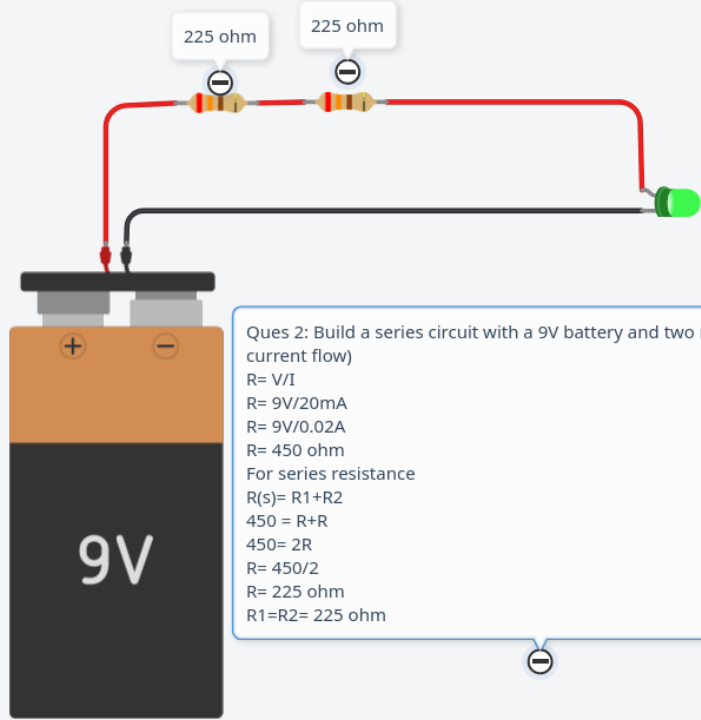

Ques 2: Build a series circuit with a 9V battery and two resistors (20mA current flow)

$R = V/I$

$R = 9V/20mA$

$R = 9V/0.02A$

$R = 450 \text{ ohm}$

For series resistance

$R(s) = R1 + R2$


$450 = R + R$


$450 = 2R$

$R = 450/2$

$R = 225 \text{ ohm}$

$R1 = R2 = 225 \text{ ohm}$

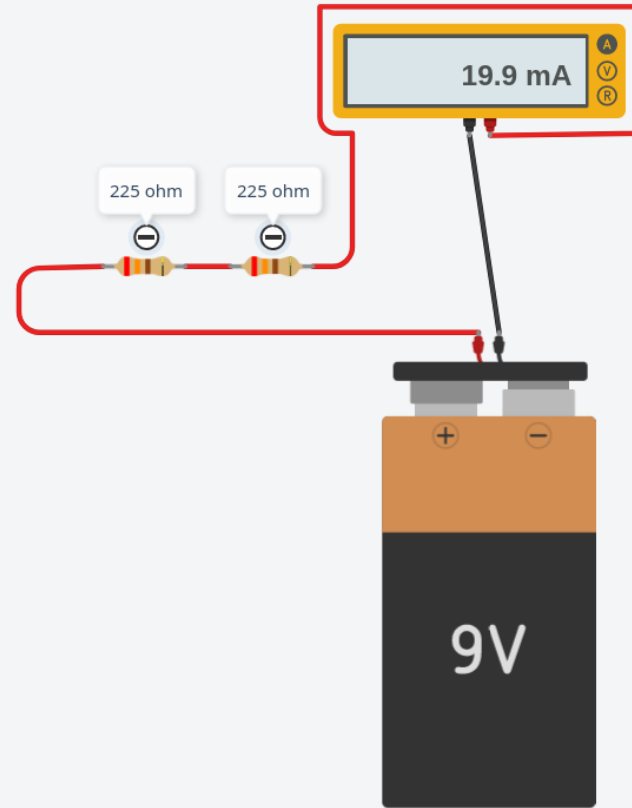

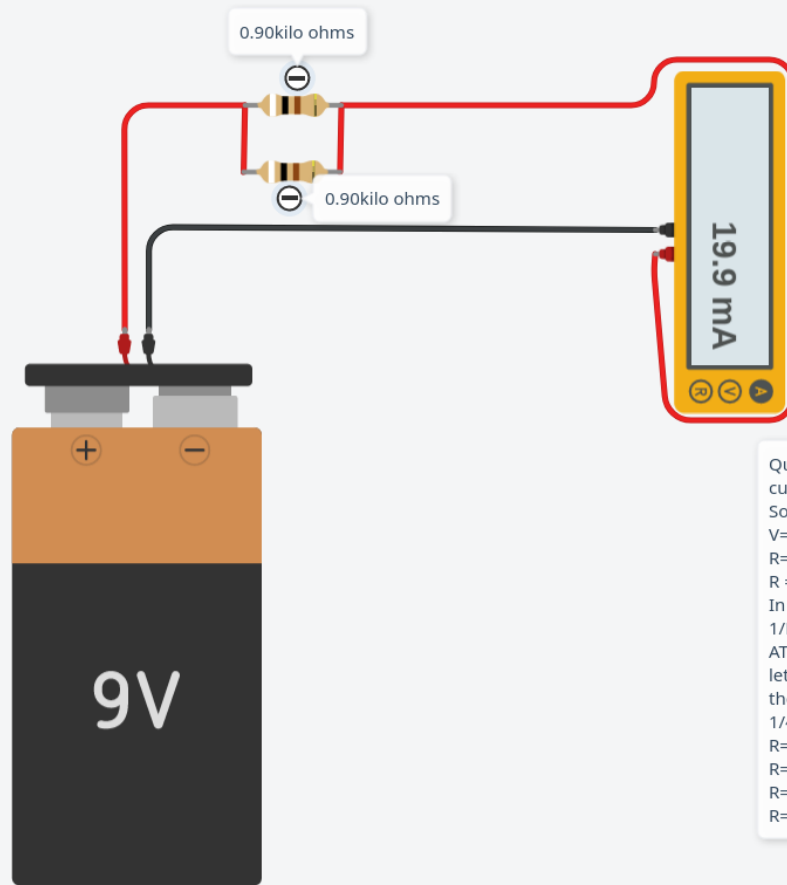

Ques 3: build a parallel circuit with a 9V battery and 2 resistors (20mA current flow).
 Solution:
 $V=9V$ and $I = 20mA$ or $0.02A$
 $R = V/I = 9V/0.02A$
 $R = 450 \text{ ohm}$
 In parallel circuit, the resistance is calculated as
 $1/R(p) = (1/R1) + (1/R2) + \dots$ so on
 ATQ, we have to build a parallel circuit and by using two resistance are R
 then, $1/R(p) = 1/R + 1/R$
 $1/450 = 2/R$
 $R = 450 * 2$
 $R = 900 \text{ ohm}$
 $R = 0.90 \text{kilo ohms}$
 $R = R1 = R2 = 0.90 \text{kilo ohms}$

Components Basic

multimeter

125.0 mA

Multimeter

Starters



Resistors



Ceramic Capacitor



Polarized Capacitor



Zener Diode



Inductor



Phototransistor